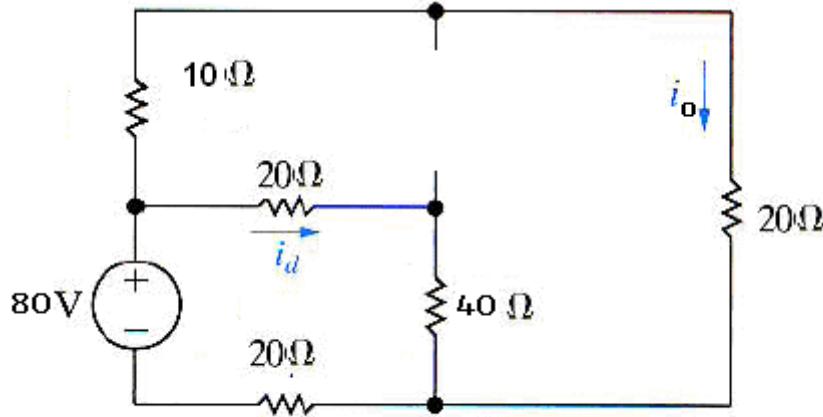


**EE 210 Quiz#2**

Name \_\_\_\_\_


---



Calculate the current  $i_o$  for the circuit above using mesh current analysis.

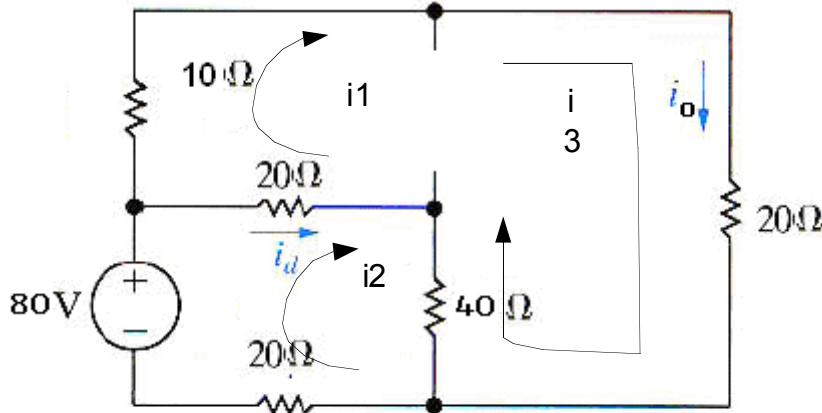**Solution:**

Supermesh , dependent source may be taken out.



KVL for two loops:

**L1: loop with 80 V source:**

$$80 - (20 + 40 + 20) i_2 + (20) i_1 + (40) i_3 = 0$$

$$i_1 - 4i_2 + 2i_3 = 4 \quad (1)$$

**L2:**

$$(20 + 10) i_1 + (20 + 40) i_3 - (20 + 40) i_2 = 0$$

$$30 i_1 + 60 i_3 - 60 i_2 = 0$$

$$i_1 + 2i_3 - 2i_2 = 0 \quad (2)$$

Finally current source equation:

$$i_3 - i_1 = 0.5 \quad i_d = 0.5(i_2 - i_1)$$

$$i_1 + i_2 - 2i_3 = 0 \quad (3)$$

Solving 3 equations simultaneously,

$$i_1 = -1A, \quad i_2 = -2A, \quad i_3 = -1.5A.$$

$$i_o = i_3 = -1.5A.$$

A minus sign of the current means the current flows reverse of the orientation we choose.